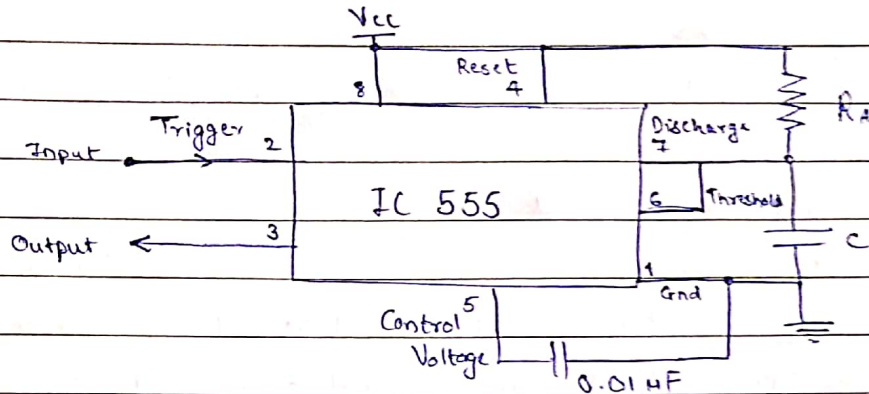


Assignment : IC 555

Q1. Design a monostable multivibrator using IC 555 for pulse width of 10 Msecs.

⇒



We know that, $t_p = 1.1 \times R_A \times C$

Let $C = 10 \text{ nF}$


$$\therefore 10 \text{ Msec} = 1.1 \times R_A \times 10 \text{ nF}$$

$$\text{i.e. } R_A = \frac{1}{1.1 \times 10^{-3}} = 909.09 \Omega$$

$$\therefore R_A = 909 \Omega, C = 10 \text{ nF}$$

2. Design an astable multivibrator for output of frequency 5 kHz and duty cycle 40%.

⇒

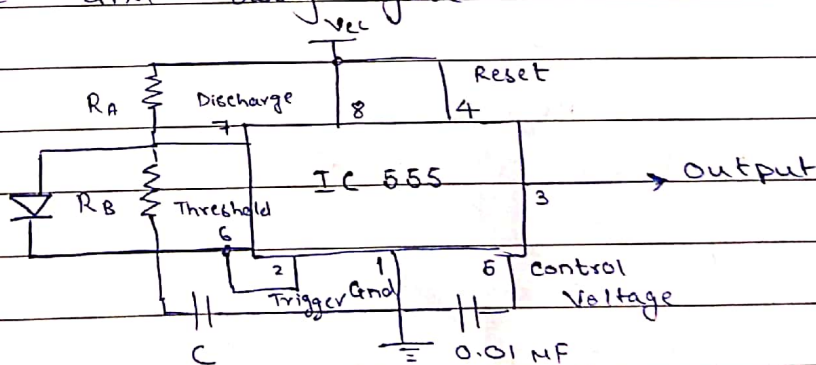

$$\text{We know that } f_0 = \frac{1.45}{(R_A + 2R_B)C} \quad \text{i.e. } 5 \times 10^3 = \frac{1.45}{(R_A + 2R_B)C}$$

$$\text{Let } C = 0.1 \mu\text{F}, \therefore R_A + 2R_B = 2900 \Omega$$

$$\text{also } \% \text{ duty cycle} = \frac{R_A + R_B}{R_A + 2R_B} \times 100 \quad (\text{for } < 50\%)$$

$$\text{i.e.} \quad 40 = \frac{R_A + R_B}{2900} \times 100$$

$$\text{i.e.} \quad R_A + R_B = 1160 \, \Omega$$

$$\therefore R_B = 1.74 \, \text{k}\Omega, \quad R_A = 1.16 \, \text{k}\Omega, \quad C = 0.1 \, \mu\text{F}$$

3. List few applications of IC 555.

- ⇒
- Used to provide accurate time delays.
 - Used for Duty Cycle oscillations of all range.
 - Used as monostable and astable vibrators.
 - Used in analog frequency meters.
 - Used for generation of PWM and PPM.
 - Temperature measurement and control devices.

4. Calculate ON time, OFF time, duty cycle and frequency of output generated by an unstable multivibrator using resistors $R_A = 5 \, \text{k}\Omega$, $R_B = 5 \, \text{k}\Omega$, $C = 10 \, \mu\text{F}$

⇒ We know that,

$$t_{\text{ON}} = 0.69 (R_A + R_B) C$$

$$= 0.69 (5 + 5) \times 10 \times 10^{-6} \times 10^3$$

$$t_{\text{ON}} = 0.069 \, \text{sec}$$

$$t_{\text{OFF}} = 0.69 (R_B) C$$

$$= 0.69 \times 5 \times 10^3 \times 10 \times 10^{-6}$$

$$t_{\text{OFF}} = 0.0345 \, \text{sec}$$

$$\therefore t_{\text{total}} = 0.1035 \, \text{sec}$$


$$\therefore f = \frac{1}{t_{\text{total}}} = 9.66 \, \text{Hz}$$

$$\therefore \% \text{ Duty cycle} = \frac{R_A + R_B}{R_A + 2R_B} \times 100 = \frac{10}{15} \times 100$$

$$= 66.67 \, \%$$

Assignment : Waveform Generator & Filters.

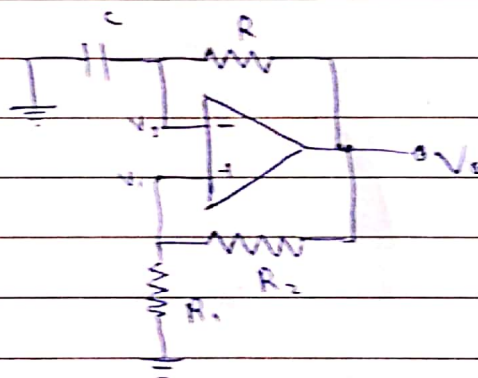1. The expression for time period of a square wave generator is $T = 2RC \ln \left[\frac{(2R_1 + R_2)}{R_2} \right]$
2. Triangular wave is derived from square wave generator by connecting integrator at the output.
3. Design a square wave generator to produce a perfect wave of 50% duty cycle with an output frequency equal to 1kHz using IC 741. Assume feedback factor to be 0.05



$$\text{Feedback factor} = 0.05 = \frac{R_1}{R_1 + R_2}$$

$$\therefore 0.05 R_2 = 1.05 R_1$$

$$\therefore R_2 = 21 R_1 \quad \therefore \text{Let } R_1 = 1k\Omega \quad \therefore R_2 = 21k\Omega$$


$$f = 1kHz = \frac{1}{2RC \ln \left(\frac{2R_1 + R_2}{R_2} \right)}$$

$$\therefore 1kHz = \frac{1}{2RC \ln \left(\frac{2+21}{21} \right)} = \frac{10.99}{2RC}$$

$$\text{Let } C = 1\mu F \quad \therefore R = \frac{10.99}{2 \times 10^3 \times 10^{-6}} = 5.495k\Omega$$

As charging and discharging time of capacitor is same
 \therefore % duty cycle = 50% , $R_1 = 1k\Omega$, $R_2 = 21k\Omega$, $R = 5.495k\Omega$, $C = 1\mu F$

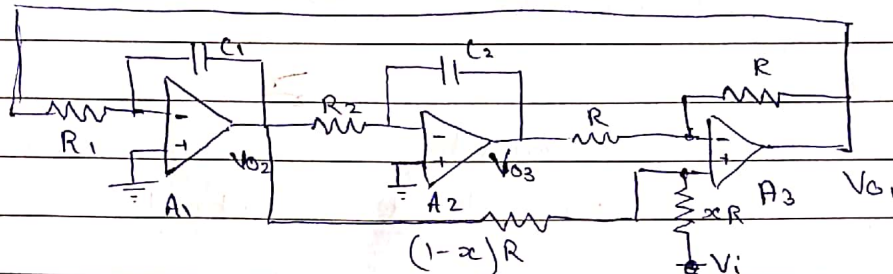4. For the circuit shown, compute transfer functions of V_{o1}/V_i , V_{o2}/V_i , V_{o3}/V_i



for A_1 , $V_{o2} = -\frac{1}{sR_1C_1} V_{o1}$

for A_2 , $V_{o3} = -\frac{1}{sR_2C_2} V_{o2} = \frac{1}{s^2(R_1C_1)(R_2C_2)} V_{o1}$

A_3 can be seen as a summing amplifier,

At node V_1 , $I_1 + I_2 = I_{b1} \approx 0$

$$\therefore \frac{V_{o2} - V_1}{(1-x)R} + \frac{V_i - V_1}{xR} = 0$$

$$\therefore V_1 = x V_{o2} + (1-x) V_i$$

similarly at node V_2 , $\frac{V_{o1} - V_2}{R} + 0 = \frac{V_1 - V_2}{R}$

$$\text{i.e. } V_2 = \frac{(V_{o1} + V_{o3})}{2}$$

As $V_1 = V_2$ (Virtual short)

$$\therefore x V_{o2} + (1-x) V_i = (V_{o1} + V_{o3})/2$$

$$\text{i.e. } -\frac{x}{sR_1C_1} V_{o1} + (1-x) V_i = \frac{V_{o1}}{2} + \frac{V_{o1}}{2s^2(R_1C_1)(R_2C_2)}$$

$$\therefore \frac{V_{o1}}{V_i} = \frac{(1-x) [2s^2(R_1C_1)(R_2C_2)]}{s^2(R_1C_1)(R_2C_2) + 2x s(R_2C_2) + 2}$$

$$\therefore \frac{V_{o2}}{V_i} = \frac{-(1-x) [2sR_2C_2]}{s^2(R_1C_1)(R_2C_2) + 2x s(R_2C_2) + 2}, \quad \frac{V_{o3}}{V_i} = \frac{(1-x)}{s^2(R_1C_1)(R_2C_2) + 2x s(R_2C_2) + 2}$$

5. Resonant frequency = 6.26 kHz